

# SIMPLE TONE CONTROL CIRCUIT

## Bass and Treble, Cut and Lift

By E. J. JAMES, B.Sc.

THE tone control system described here has the merit of requiring only resistors and capacitors. As a result it is unusually easy to fit to an existing amplifier, particularly as the absence of an inductance reduces the likelihood of trouble from hum pick-up.

While the circuit does not give the large amounts of lift which can be obtained by more complicated designs or by the use of resonating circuits, it is sufficient for normal requirements. The bass lift is not intended to compensate for the falling record characteristic below 300 c/s. This

distortion consists of the introduction of frequencies 2, 3, 4, etc., times the fundamental frequency, a rising frequency characteristic emphasizes any which is present in the signal prior to the tone-control stage. The higher order harmonics, which are the most disturbing to the ear, are the ones which receive the greatest amplification. This limit to the useful degree of top lift applies to all forms of top lift circuit, and is inherent.

The basic bass-lift circuit is shown in Fig. 1(a). The capacitor  $C_1$  has a reactance which increases as the frequency decreases, so that the output increases at lower frequencies. By shunting it with a variable resistor, Fig. 1(b), the degree of bass lift can be controlled. In the same way Fig. 2(a) shows the circuit for bass cut, and in Fig. 2(b) a variable resistor controls the amount of bass cut.

The two circuits of Figs. 1(b) and 2(b) can now be combined to give that of Fig. 3, where bass lift

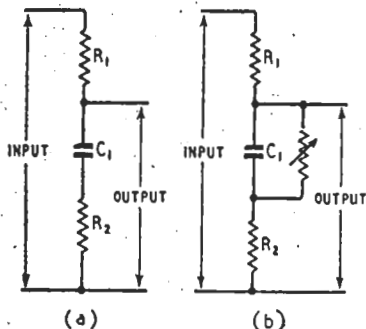


Fig. 1. The basic bass lift circuit is shown at (a). The lift is controllable by a variable resistor (b).

should be dealt with separately, so allowing the tone control to give extra lift for records abnormally deficient in bass or for listening at low volume. If required, however, a fair measure of compensation can be obtained.

It is not always realized that large amounts of bass lift cannot be achieved in a simple single-stage non-resonating circuit without lifting the lower middle register as well. The maximum rate of lift is fixed and it is only by starting at a higher frequency that greater lifts can be obtained. The amount of top lift which can be satisfactorily used is limited by amplitude distortion. Since this

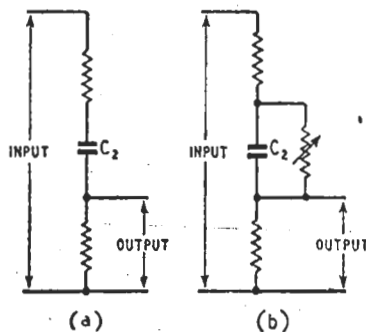


Fig. 2. Bass cut can be obtained with this circuit (a) and is controllable by a variable resistor (b).

and cut are controlled by the potentiometer  $R_3$ .

Fig. 4(a) shows a circuit giving top lift. Here the reactance of the capacitor  $C_3$  decreases as frequency increases, so that the output rises with frequency. In this case a variable resistor in

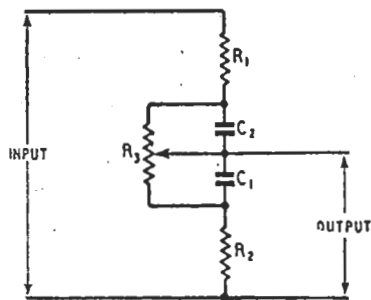


Fig. 3. This diagram shows the bass cut and lift circuits combined and controlled by the potentiometer  $R_3$ .

series with  $C_3$ , as shown in Fig. 4(b) gives control of top lift.

Similarly Figs. 5(a) and 5(b) show top cut and controlled top cut respectively. Once more the two circuits can be combined, Fig. 6, to give control of top lift and top cut by means of the potentiometer  $R_4$ .

The treble and bass controls can now be combined into the circuit shown in Fig. 7, and will normally be used as part of the coupling between two valves. For signal current the resistance,  $R_1 + R_2$ , is in parallel with the anode load resistance of the previous valve.  $R_1$  and  $R_2$  should therefore be as high as possible so that the valve does not work into too low a load. The minimum load should be about twice the valve impedance. On the other hand they must not be too high or the valve output capacitance and stray capacitances will affect response at high frequencies.

A simple method of finding

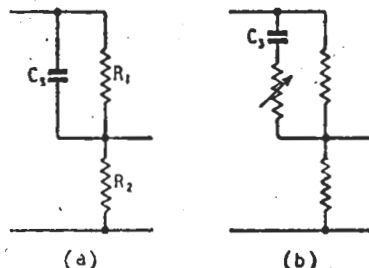


Fig. 4. Top lift is given by this basic arrangement (a) and can be varied by a series resistor (b).

COVER

erected by the G.E.C. on the sites  
row, Dunstable, Byfield and Rowley  
ingham television link. These masts,  
used for the initial working of the  
ected towers have been built. This  
the mast at Harrow. The smaller  
signal can be transmitted direct from  
y during tests, thus avoiding routing  
terminal station in London.

should remember to correct S meter  
readings for the displacement due to  
the local b.f.o., which does affect  
the a.v.c. characteristic of most re-  
ceivers, however well designed they  
may be.

Instead of a modulation report, a  
c.w. operator might welcome a few  
words on his keying characteristic  
by a nearby reporting station.

In testing with a receiving sta-  
tion if the first S meter reading is  
taken as an arbitrary level, then im-  
mediate subsequent readings are of  
a definite value to a transmitter  
making test adjustments and assess-  
ing their effect on the radiated  
signal. H. HARDY, G4GB.

Ruislip, Middx.

Long-delay Relay Circuit

THIS circuit, described in your  
February issue, works well in  
practice, and I have used it for a  
year or more. The best results are  
obtained by using a high-slope triode  
having a short grid base, and I have  
recently found that an EC9r (mini-  
ature triode) used with C=2 mfd.  
and R=3.3 megohms will easily en-  
able a 5-minute time delay to be  
attained.

A similar result can be obtained  
by connecting R<sub>c</sub> in the anode in-  
stead of the cathode circuit of the  
valve, and C from anode to grid,  
instead of grid to h.t. negative.

Whichever circuit arrangement be  
used, the time constant CR becomes  
effectively multiplied by the ampli-  
fication factor. If any of your  
readers are seeking more information  
they might be interested in an article  
by the writer published in *The En-  
gineer* of 29th October, 1948, in  
which these circuits are described  
and analyzed. J. H. LUCAS.

Mullard Electronic Research  
Laboratory.

"Simple Tone Control  
Circuit"

I SHOULD like to draw your atten-  
tion to the fact that a tone-con-  
trol circuit exactly similar to that  
described by E. J. James in your  
February issue, except for the slight  
differences in values of elements,  
was designed by our engineer

Michael Volkoff as early as July,  
1939, when the first amplifier em-  
bodying this circuit was built. We  
have used this circuit ever since  
then, and there are now over one

thousand amplifiers in Belgium with  
this tone control built in.

WILLY L'HOEST,  
Rocke International, Ltd.  
Brussels.

SENSITIVE ELECTRONIC RELAY


R.F. Oscillator Controlled by External Capacitance

A RANGE of electronic units de-  
signed for industrial use and  
functioning on the principle that the  
proximity of a substance, whether  
solid, liquid or a gas, trips a relay  
has been introduced by Fielden  
(Electronics) Ltd., Holt Town  
Works, Manchester, 10.

The tripping of the relay can be  
utilized to perform a variety of  
functions, for example, counting the  
number of items passing a given  
point, giving warning when the level

the circuit is set up to be in an  
oscillating state, the proximity of a  
body, liquid or gas to the remote  
electrode will stop oscillation. Con-  
versely, it can be made to start  
oscillation.

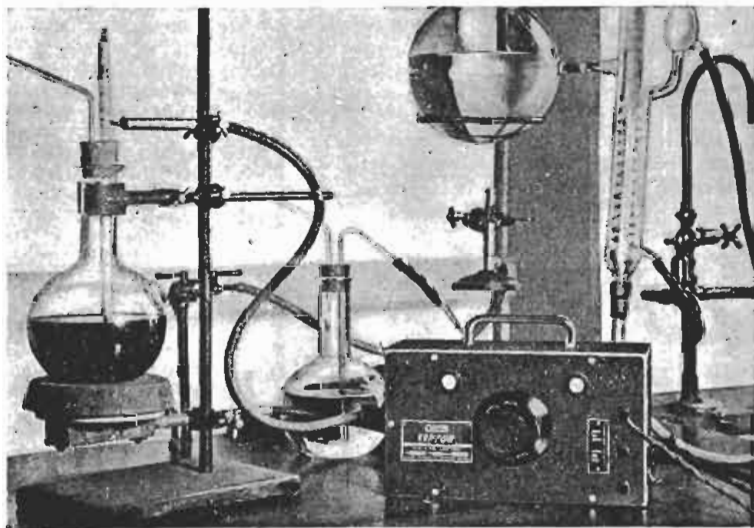The behaviour of the oscillator is  
easily utilized for any number of  
functions, mechanical or electrical,  
by rectifying the radio frequency or  
even using the change in anode cur-  
rent between the oscillating and  
non-oscillating state.



Fielden Tektor proximity switch attached to a thermometer and arranged to give remote warning when a liquid reaches a pre-determined temperature.

of a liquid has reached or fallen  
below a certain level, or, alter-  
natively, to operate mechanism to  
stop or start the flow of liquid.  
Many other applications will suggest  
themselves.

In the case of objects, it is not  
necessary that they be conductors,  
and the devices will be actuated by  
any body of a reasonable size, be it  
jam-jars, biscuits, bricks, motor  
cars or people.

The apparatus is known as the  
"Tektor" and consists of a valve  
oscillator with a capacitance bridge  
in the feedback circuit and arranged  
so that a change of capacitance at  
the end of a cable joined to the  
bridge reverses the phase of the  
oscillator feedback voltage. Thus if

At present the Tektor is available  
in four different forms, a proximity  
switch, a proximity counter, a  
double Tektor for recording move-  
ment in two directions such as high  
and low levels of liquid in a con-  
tainer, and a meter relay which is  
actuated by current or voltage read-  
ings on an indicating meter. This  
unit has an additional pointer on  
the meter which can be moved to  
any part of the scale and when the  
normal indicating pointer comes  
opposite the fixed pointer the elec-  
tronic relay is actuated and can be  
made to sound an alarm.

The apparatus operates from the  
a.c. supply mains and consumes be-  
tween 20 and 25 watts according to  
the functions required.

# Negative-Feedback Tone Control

By P. J. BAXANDALL

B.Sc.(Eng.)

## Independent Variation of Bass and Treble Without Switches

THE circuit to be described is the outcome of a prolonged investigation of tone-control circuits of the continuously-adjustable type, and provides independent control of bass and treble response by means of two potentiometers, without the need for switches to change over from "lift" to "cut." Unusual features are the wide range of control available, and the fact that a level response is obtained with both potentiometers at mid-setting. The treble-response curves are of almost constant shape, being shifted along the frequency axis when the control is operated, and there is practically no tendency for the curves to "flatten off" towards the upper limit of the audio range. The shape of the bass-response curves, though not constant, varies less than with most continuously-adjustable circuits.

**The "Virtual-Earth" Concept.**—The performance outlined above has been achieved by the use of a negative-feedback circuit instead of the more usual passive type of network<sup>1,2</sup> and it is desirable that the reader should become familiar with the "virtual-earth" concept<sup>3</sup> as applied to feedback amplifiers, before the operation of the tone-control circuit is considered in detail. The idea behind this concept is quite simple, and may be explained with reference to Fig. 1, in which all irrelevant details such as blocking capacitors, grid bias, etc., have been omitted, and in which  $V_{in}$  and  $V_{out}$  refer to a.c. components only. If the input resistor,  $R_{in}$ , is made equal to the feedback resistor,  $R_{fb}$ , then the circuit becomes the well-known "see-saw" or "anode-follower" phase-splitter,<sup>4,5</sup> and gives an output voltage which is 180 degrees out of phase with the input voltage and of slightly smaller magnitude. Now the a.c. voltage at the grid is equal to the output voltage divided by the valve gain, which may be 100 or more if the valve is a pentode, so that for many purposes the grid voltage is negligibly small in comparison with  $V_{in}$  and  $V_{out}$ . By thus neglecting the grid voltage, the following approximate relationships may be immediately deduced:—

$$I_{in} \doteq V_{in}/R_{in} \quad \dots \dots \dots (1)$$

$$I_{fb} \doteq V_{out}/R_{fb} \quad \dots \dots \dots (2)$$

where  $I_{in}$  and  $I_{fb}$  are as shown in Fig. 1.

If grid current in the valve is also negligible, which is normally the case, the application of Kirchhoff's first law (or just common sense!) to the junction of  $R_{in}$  and  $R_{fb}$  gives  $I_{in} + I_{fb} = 0$ , so that, from (1) and (2):—

$$\begin{aligned} V_{in}/R_{in} + V_{out}/R_{fb} &\doteq 0 \\ \text{i.e., } V_{out}/V_{in} &\doteq -R_{fb}/R_{in} \quad \dots \dots \dots (3) \end{aligned}$$

When the grid voltage is neglected in this way, the grid is often called a "virtual-earth" point, and the use of this concept, though not necessary for dealing with a simple circuit such as Fig. 1, is found to be very helpful when dealing with more elaborate arrangements, and frequently gives one a far clearer physical picture of what is going on than does a straightforward mathematical analysis. The great practical value of this method of approach appears to have been first fully appreciated by Professor F. C. Williams, who also introduced the name "virtual earth."

**Treble-Lift Circuit.**—The basic circuit used for obtaining treble lift is shown in Fig. 2, in which the potentiometer P is made of sufficiently low resistance to ensure that the voltage at its slider, when the latter is at the middle of the element, is not appreciably affected by the current supplied to C even at the top end of the audio range. Let  $k$  be the fraction of the total potentiometer resistance lying between the slider and earth; then the total input current,  $I_{in}$ , flowing towards the virtual earth, is  $I_1 + I_2$ , where  $I_1$  is approximately  $V_{in}/R_{in}$  and  $I_2$  is approximately  $jkV_{in}\omega C$ . The feedback current,  $I_{fb}$ , is approximately  $V_{out}/R_{fb}$  and the application of Kirchhoff's first law to the virtual-earth junction gives  $I_1 + I_2 + I_{fb} = 0$  and hence the relationship:—

$$\begin{aligned} V_{in}/R_{in} + jkV_{in}\omega C + V_{out}/R_{fb} &\doteq 0 \\ \text{which may be rearranged in the form:—} \\ V_{out} &\doteq -V_{in}(R_{fb}/R_{in} + jk\omega CR_{fb}) \quad \dots \dots (4) \end{aligned}$$

It will be seen later that in order to combine this treble-lift circuit in a satisfactory manner with the treble-cut circuit,  $R_{fb}$  should be made equal to  $R_{in}$ ; then, using R in place of these symbols, equation (4) becomes:—

$$V_{out} \doteq -V_{in}(1 + jk\omega CR) \quad \dots \dots (4a)$$

The output voltage may thus be regarded as having two components, one of which is independent of frequency (for a constant value of  $V_{in}$ ), whereas the other one, leading in phase by 90 degrees as indicated by the operator "j," has its magnitude proportional

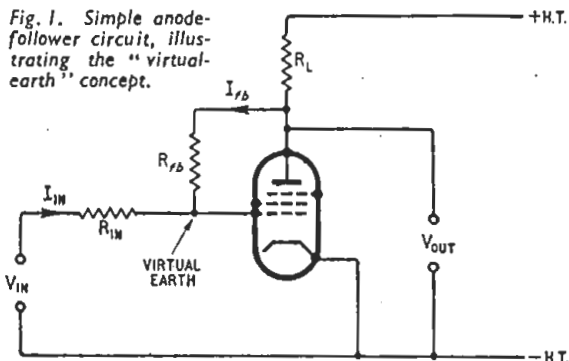


Fig. 1. Simple anode-follower circuit, illustrating the "virtual-earth" concept.

<sup>1</sup> "Getting the Best from Records—Part III" by P. G. A. H. Voigt, *Wireless World*, April 1940.  
<sup>2</sup> "Simple Tone Control Circuit" by E. J. James, *Wireless World*, Feb. 1949.  
<sup>3</sup> Section 2.5 of "Waveforms," Book 19 of Radiation Laboratory Series, published by McGraw-Hill.  
<sup>4</sup> "The See-saw Circuit" by M. G. Scroggie, *Wireless World*, July 1945.  
<sup>5</sup> "The Anode-Follower," by B. H. Briggs, *R.S.G.B. Bulletin*, March 1947.

used for bass lift and cut, omitting irrelevant details as before. In order to give level response with the potentiometer at mid-setting, and to allow the circuit to be easily combined with the treble-control circuit,  $R_1$  and  $C_1$  are made equal to  $R_2$  and  $C_2$ . At middle and high frequencies the potentiometer is almost "shorted out" by the low reactances of  $C_1$  and  $C_2$ , so that the circuit becomes almost the same as Fig. 1 with  $R_{in} = R_{ob}$  and a gain of approximately unity is obtained. As the frequency is lowered, the gain gradually rises or falls towards an asymptotic level determined by the potentiometer setting; and, as with the treble-control circuit, the response curves are approximately mirror images in the 0 db line for equal potentiometer displacements either side of the level-response setting.

The amount, in decibels, by which the gain of the Fig. 5 circuit departs from unity, is given approximately by:—

$$\text{Lift, in db} = 20 \log \left| \frac{Z_{ob}}{Z_{in}} \right| \quad \dots \quad (6)$$

where  $|Z_{in}|$  and  $|Z_{ob}|$  are the moduli of the impedances between input terminal and grid and between anode and grid respectively. (Note, if an impedance calculated by means of the "j" notation comes out to  $R + jX$ , the modulus, or magnitude, is  $\sqrt{R^2 + X^2}$ ; see reference (6).) Equation (6) may be used to calculate the response curves, point by point, for various potentiometer settings—a straightforward though time-consuming process! The "cross-over" effect noticeable with some of the measured bass curves shown in Fig. 8 may seem surprising at first, but it is quite genuine and equation (6) gives just the same result.

**Complete Tone Control.**—Fig. 6 shows the final circuit evolved, which is, effectively, a combination of the treble and bass circuits described above. There is, however, one point about the relation between Fig. 6 and the previous circuits which may need some explanation. At middle and high frequencies, where  $C_1$  and  $C_2$  in Fig. 6 may be regarded as short-circuiting the potentiometer  $P_1$ , the relevant part of

the circuit becomes as shown in Fig. 7(a). It will be seen that the three resistors  $R_1$ ,  $R_2$  and  $R_3$  are connected in "star" between the three points A, B and C. Now it is well known that, as far as the external circuit is concerned, three resistors in "star" are exactly equivalent to three resistors, of suitably different values, connected in "delta" so that Fig. 7(a) is equivalent to Fig. 7(b). In Fig. 7(b), the presence of  $R_c$  cannot appreciably affect the frequency response, because the resistance is between two points A and B both of which have a relatively low impedance to earth (point A, since the source of input voltage is assumed to be of low impedance; and point B, because it is the output terminal of an amplifier having voltage negative feedback). Hence, ignoring  $R_c$  for the above reason, Fig. 7(b) is equivalent to a combination of the treble lift and cut circuits of Figs. 2 and 4, and therefore Fig. 7(a) is also equivalent to this combination. The relation between star and delta networks is such that if  $R_1$  is made equal to  $R_2$  in Fig. 6, which is essential for giving "mirror image" lift and cut curves, then  $R_a$  and  $R_b$  in Fig. 7(b) are each equal to  $R_1 + 2R_3$ . The important practical result of this reasoning is that the treble response will be 3 db up or down, at full-lift or full-cut settings respectively, at the frequency for which the reactance of  $C_3$  in Fig. 6 is numerically equal to  $R_1 + 2R_3$ .

The values of the main components in Fig. 6 were decided as follows.  $P_1$  was fixed at 1 M $\Omega$ , this being considered the highest really desirable value for a carbon potentiometer. To give about 20 db asymptotic bass lift and cut, the nearest standard value for  $R_1$  and  $R_2$  was 100 k $\Omega$ . A suitable compromise for  $C_3$  was 100 pF, on the grounds that, to obtain a result in accordance with calculation, the value should be large in relation to likely wiring strays, but that too large a value would result in an undesirably low impedance being thrown across the source of  $V_{in}$ . The value of  $P_2$  then had to be chosen so that, with the slider half way between the centre-tap and one end the effective internal resistance of the potentiometer, regarding it as a generator feeding  $C_3$ , should be not more than, say, half the reactance of  $C_3$  at 10 kc/s. Now the reactance of 100 pF at 10 kc/s is

\* "What it is and How to Use it," by Cathode Ray, *Wireless World*, February 1948.

\* "Electric Circuits and Wave Filters," by A. T. Starr, p. 80 published by Pitman.

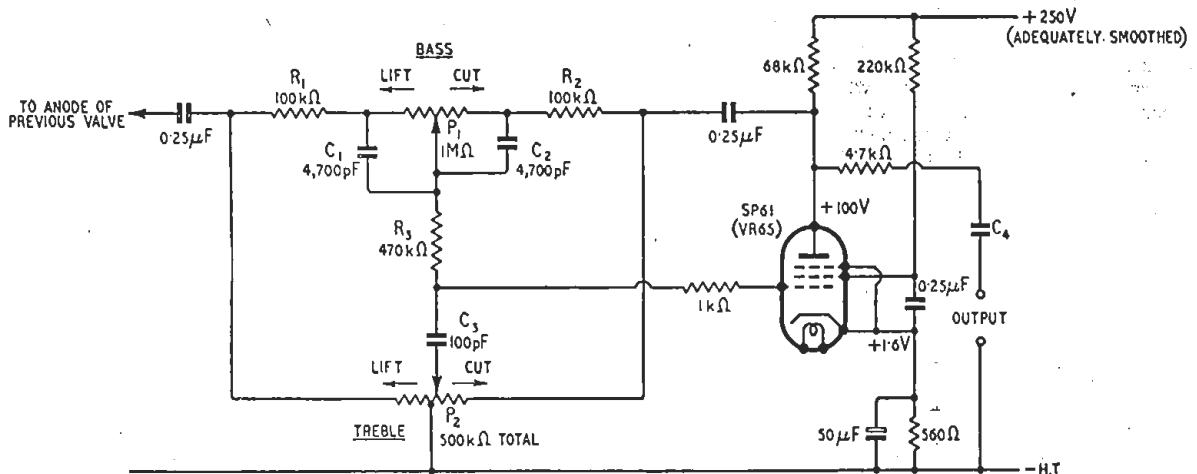


Fig. 6. The complete tone-control circuit.  $R_1$ ,  $R_2$ ,  $C_1$ ,  $C_2$ ,  $R_3$  and  $C_3$  should preferably be within 5 per cent of marked values.  $P_1$  and  $P_2$  is Dubilier Type 'C' control, 500k $\Omega$ , with fixed tapping at 50 per cent rotation.  $C_4$  should normally be 0.05 $\mu$ F if following stage has 250-k $\Omega$  grid-leak.

# Aerial Exchange


*Switching on the Grand Scale for Ten Radio Transmitters and Twenty Aerials*

**P**RACTICAL effect has recently been given at one of the Admiralty's high-power transmitting stations to a requirement calling for elaborate planning and precision engineering. This requirement was to provide a reasonably simple scheme for connecting any one of 10 radio transmitters to any one of 20 different aerial systems. Some are rhombics, others dipoles, but all have one common feature which is that 600-ohm balanced open-wire transmission lines are used.

The main problems were to provide a way of switching which would not disturb the characteristic impedance of any of the lines and to handle 25 kW of r.f. power. Changeover is not carried out with power on the lines.

The switching system is partially motorized and consists of a large semi-circular structure of 14 ft radius and some 16 ft high. This is fitted with 11 horizontal rails and between each pair is a movable carriage. Each carriage is driven by a small electric motor through flexible shafting and they can be traversed from end to end of the structure. There are 10 such

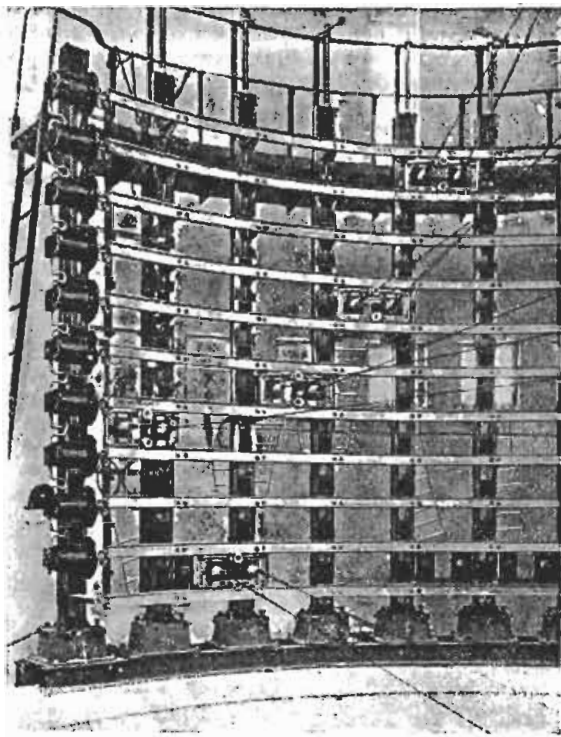*Part of the aerial exchange switching frame. Horizontal traversing motors are stacked on the left and a few of the hand winders for the vertically moving carriages are seen round the top gallery. Aerial feeders are just visible in the background.*



carriages and their driving motors can be seen stacked on the left of the illustration.

Similar carriages, but travelling vertically between the upright pillars, are mounted at the back of the structure. There are 20 of these and they are moved up or down by hand-operated lead-screws, the controls for which are arranged round a gallery at the top of the framework.

Each carriage, vertical and horizontal, is fitted with two large insulators having on their inner faces domed-shaped contact studs. The spacing is exactly 10-in which is the same as that of the transmission lines.

From a vertical column located at the exact centre of the system is taken a two-wire transmission line to each of the horizontally moving carriages. These lines are under spring tension and remain taut at all positions of the carriages. From this column the feeders pass into the transmitting hall and thence to the various transmitters.

Similarly, to each vertically moving carriage is brought, through a separate window in the outer wall of the building, a 600-ohm transmission line from one of the aerials; there are 20 in all and some of the lines can be seen in the illustration draped from the frame to the windows.

The method of switching is now fairly obvious, the carriage carrying a transmitter feeder is moved horizontally to the required aerial bay and that aerial's feeder carriage is moved up or down to bring the two sets of contacts into alignment. The rear set of insulators is on a sprung plate which ensures a firm and good electrical connection.

Initial planning of the system was carried out by the Admiralty Signal and Radar Establishment and the installation was engineered by P. & L. Miller, Ltd., of Henege Street, London, E.1.

## “Negative-feedback Tone Control”

**O**WING to an omission from the inscription to Fig. 6 of the above article in the October issue, some ambiguity has arisen regarding the law of the potentiometers  $P_1$  and  $P_2$ , though from the curves of Fig. 8 it is implicit that they are linear. The relevant part of the inscription to Fig. 6 should read “ $P_1$  and  $P_2$  must both have linear elements.  $P_2$  is Dubilier Type ‘C’ control, 500 k $\Omega$ , with fixed tapping at 50 per cent rotation.”

The dotted curves of Fig. 8 with  $P_2$  centre tap disconnected were measured with an input attenuator forming a return path for the grid. When the filter is fed via a capacitor (as in Fig. 6), and the modified response is required, the grid may be “tied down” to earth by a high-resistance leak, but the preferred method is to use two 330-k $\Omega$  resistors, one from the left-hand and the other from the right-hand end of  $P_2$  to earth, the central tap being disconnected. The lower value of resistors avoids possible trouble from leaky coupling capacitors, and/or slight grid current, without appreciably affecting feedback and non-linearity distortion.